

**SAN FRANCISCO STATE UNIVERSITY
SCHOOL OF ENGINEERING**

ENGR 206 Lab Report

Date

**Experiment # 3:
KIRCHHOFF'S LAWS**

by

Name

SAMPLE

Lab Partner:

Name

Experiment #3: KIRCHHOFF'S LAWS

Objective

To verify experimentally Kirchhoff's voltage and current laws as well as the principles of voltage and current division.

Apparatus

In this experiment, we use the following apparatus:


- Agilent E3630A Triple Output Power Supply,
- Agilent 34401A Digital Multimeter,
- 10K Ω Potentiometer, and
- a Decade

The Triple
Lab Repor
decade b


The pote
single-tu

SAMPLE

Figure #1. Types of Trimmer Potentiometers

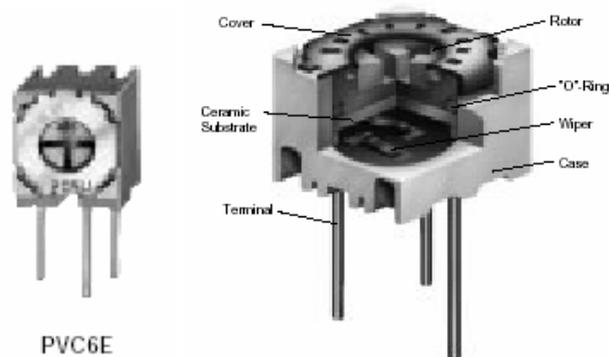

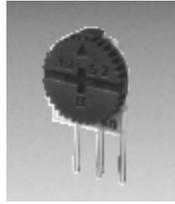a. muRata PVC6E - Lead Sealed Single-turn Potentiometer



b. Bourns 3352 - 3/8" Single-turn thumb adjustable

A potentiometer, (called "pot" for short), is a resistor with three terminals as shown in Figure # 2. The resistance between terminals A and B is fixed.

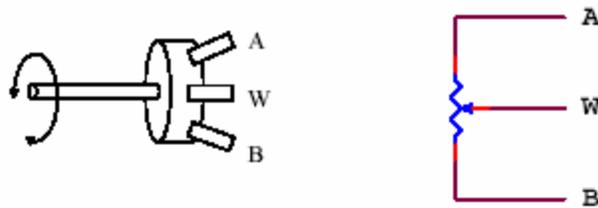


Figure #2. Potentiometer and its equivalent circuit

In our case
wiper blade
resistance
It is obvious
resistance
pot setting
Figure# 3.

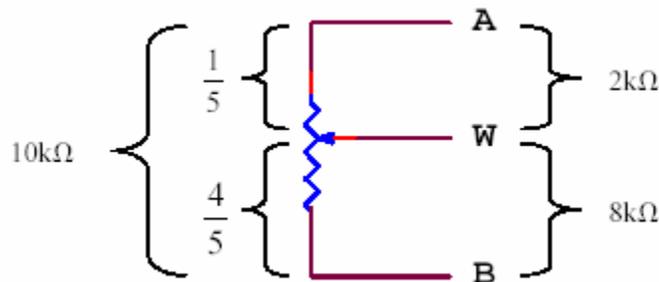


Figure #3. Equivalent circuit for the 10 kΩ potentiometer

A potentiometer can be used as a variable voltage divider or as a variable resistor. In the former case, all three terminals are used (e.g., Figure 5). In the latter case, only two terminals, W and either A or B, are used although it is a

common practice to connect the unused terminal to the wiper to eliminate possible noise pickup.

A decade box is used for accurate resistance reading. The one available in our lab has 6 decade switches to allow for 1,000,000 resistance values to be dialed.




Figure #4, The TEGAM Model DB62-XX is a DEKABOX in-line Decade Resistor.

Procedures, Data, Results and Analysis

A. Voltage Div

1. Constru

We sel

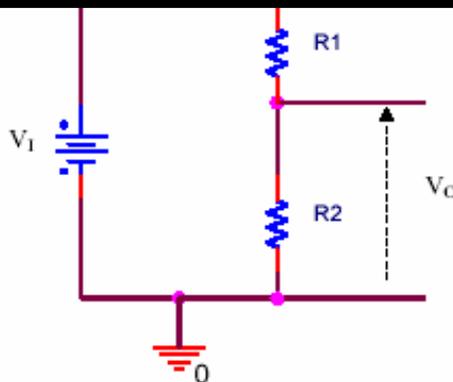

$$V_0 = V_1 \frac{R_2}{R_1 + R_2}$$

Figure #5. Voltage Divider

2. Turn the power supply on. With the help of the DC voltmeter, adjust the power supply to output +10 V.

We adjusted the power supply to output 10.0114 V.

3. Measure the voltage around the loop and verify the validity of KVL for this particular circuit. Repeat the loop measurements but with test leads reversed. Do these new readings still satisfy KVL?

Kirchhoff's Voltage Law (KVL) states that the sum of all voltages around a closed loop is zero.

The voltage measurements are:

across R1: 5.0079 V

across

across

The sum of all the
KVL is satisfied.

If we reverse the test

across

across

across source: 10.0114 V.

Again, since the sum of all voltage changes is zero (within 5% tolerance), KVL is satisfied.



4. Compare the measured V_0 with the theoretically computed V_0 . Account for causes of possible discrepancy.

We compute the value for V_0 as follows:

$$V_0 = V_I \frac{R_2}{R_1 + R_2} = 10.0114 \text{ V} \cdot \frac{1 \text{ k}\Omega}{5.0079 \text{ k}\Omega + 1 \text{ k}\Omega}$$

The measured value for V_0 is very small, within some resistance in the wires.



5. Leave R2 in place, repeat step 3 with R1=10kΩ.

CASE 1: R1=100Ω, R2=1kΩ

The voltage measurements are:

across R1:

across R2:

across source: -10.0118 V

Sum = - 0.002 V

The sum of all these voltages is close to zero (within 5% tolerance).
Therefore, KVL is satisfied.

If we reverse the test leads, we get the following readings:
across R1: 0.9101 V
across R2: 0.9101 V
across source: -10.0114 V
Sum = 0.0002 V

Again, since the sum of all these voltages is close to zero (within 5% tolerance), KVL is satisfied.

The theoretical value for V_0 is:

$$V_0 = V_I \frac{R_2}{R_1 + R_2} = 10.0114 \text{ V} \frac{0.1 \text{ k}\Omega}{0.1 \text{ k}\Omega + 1 \text{ k}\Omega} = 0.9101 \text{ V}$$

The measured value for V_0 is 0.9168 V. The discrepancy is 0.0067 V (0.7% error, within 5% tolerance). This is due to the resistance of the wires and manufacturing tolerances.

CASE 2: R1=10kΩ, R2=1kΩ

The voltage measurements are:
across R1: 9.1012 V
across R2: 0.9101 V
across source: -10.0114 V
Sum = -0.0001 V

The sum of all these voltages is close to zero (within 5% tolerance).
Therefore, KVL is satisfied.

If we reverse the test leads, we get the following readings:

across R1: 9.1012 V
across R2: 0.9101 V
across source: -10.0114 V
Sum = 0.0001 V

Again, since the sum of all these voltages is close to zero (within 5% tolerance), KVL is satisfied.

The theoretical value for V_0 is:

$$V_0 = V_I \frac{R_2}{R_1 + R_2} = 10.0114 \text{ V} \frac{10 \text{ k}\Omega}{10 \text{ k}\Omega + 1 \text{ k}\Omega} = 9.1012 \text{ V}$$

The measured value for V_0 is 9.9064 V. The discrepancy is 0.8052 V, about 8% error from the theoretical value, which is more than the 5% tolerance. It is p
measurements, s

6. Connect the 10k Ω

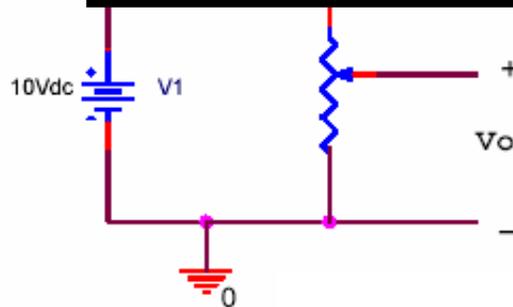


Figure #6. A Variable Voltage Divider

7. Monitor V_0 with the dc voltmeter as you rotate the pot shaft back and forth. Within what limits does V_0 vary? Why?

V_0 varies within $V_{\max} = 10.0043 V$ and $V_{\min} = 0.242 mV$. $V_{\max} = 10.0043 V$ is close to the value of $V_{\text{input}} = 10.0114 V$; the discrepancy between the two is 0.0071 (0.07% error). The minimum resistance is not zero because some minimal resistance in the pot can not be avoided.

8. Adjust the shaft position in parallel with V_0 . W
change. Compare the

The shaft position i
 $V_0 = 5.0096 V$. After
new value is: $V_0' =$
 R_2 is now replaced
parallel).

$$R_x = R_2 \parallel R_p = \frac{R_2 \times R_p}{R_2 + R_p} = \frac{50 \text{ k}\Omega}{10 \text{ k}\Omega + 5 \text{ k}\Omega} = 3.33 \text{ k}\Omega$$

$$V_o = V_I \frac{R_x}{R_1 + R_x} = 10.0114 \text{ V} \frac{3.33 \text{ k}\Omega}{3.33 \text{ k}\Omega + 5 \text{ k}\Omega} = 4.006 \text{ V}$$

The difference between
Vo”=3.9590 V (1.1% error
and human error in mani

SAMPLE

B. Current Division

1. Use the 0 to 6 volt Power Supply output and construct the voltage divider circuit as shown in Fig. 7. Turn the Power Supply voltage output to 0 volts while constructing the circuit. We will be simulating a constant current source by using a voltage source and adjusting the voltage as needed to create a predetermined current.

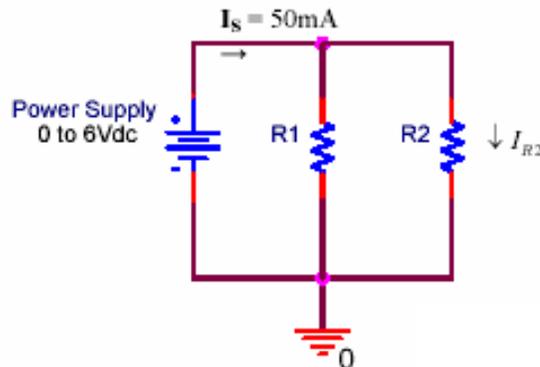


Figure #7. A Current Divider

2. Use $R1 = R2 = 100\Omega$.

The resistors we use have 5% tolerance level (gold band).

3. Watching the display of the Power Supply, adjust the current I_s until it reaches 50mA.

We adjusted the current to 50.139 mA DC. This gives us 0.139 mA error in measurements (0.3%) we should consider when explaining discrepancy later.

4. With the use of the DC ammeter verify KCL by measuring the current I_{R2} through the resistor R_2 .

Kirchhoff's Current Law (KCL) states that the sum of all currents for any node is zero.

$$\begin{aligned} I_s &= 50.139 \text{ mA} \\ I_{R2} &= -26.296 \text{ mA} \\ \frac{I_{R2} \times R_2}{R_1} &= \dots \\ \text{Sum} &= \dots \end{aligned}$$

This is close to zero, the discrepancy is due to the wires or bad connections.



5. Using the principle of current division calculate the theoretical value of I_{R2} and compare it with the measured value. Account for the causes of possible disagreements.

$$I_{R2} = I_I \frac{R_2}{R_1 + R_2} = 50.139 \text{ mA} \frac{100 \Omega}{100 \Omega + 100 \Omega} = 25.0695 \text{ mA}$$

The measured value is $I_{R2} = 26.296 \text{ mA}$. The discrepancy is 1.226 mA (4.5% error), within 5% tolerance. This disagreement is possibly due to inaccuracy in measurement apparatus and resistor tolerances.

6. Leave R_2 in place, repeat steps 4 and 5 for the case $R_1 = 10 \Omega$ and for the case $R_1 = 1 \text{ k}\Omega$. Be sure to maintain the same supply display.

CASE 1: $R_1 = 10 \Omega$, $R_2 = 100 \Omega$

$$\begin{aligned} I_s &= -50.312 \text{ mA} \\ I_{R2} &= 6.88 \text{ mA} \\ I_{R1} &= 47.2 \text{ mA} \\ \text{Sum} &= -3.23 \text{ mA} \end{aligned}$$



This is close to zero, within tolerance. Hence, KCL is satisfied. The discrepancy is due to the inaccuracy of the measuring equipment and resistance tolerance.

$$I_{R2} = I_I \frac{R_1}{R_1 + R_2} = 50.312 \text{ mA} \frac{10 \Omega}{10 \Omega + 100 \Omega} = 4.573 \text{ mA}$$

There is a discrepancy of 2.31 mA (50% error). This error is too high to be explained simply by the resistor tolerances or resistance in wires. (For example, even if we take that the actual resistor value is 95 Ω instead of 100 Ω , and plug-in exactly 50mA in the formula, the error goes down to 40%)
There is a possibility we made an error in this measurement.

CASE 2: R1=1k Ω , R2=100 Ω

$$\begin{aligned} I_s &= -50.151 \text{ mA} \\ I_{R2} &= 45.66 \text{ mA} \\ I_{R1} &= 4.821 \text{ mA} \\ \text{Sum} &= 0.33 \text{ mA} \end{aligned}$$

This is close to zero, within 5% tolerance. Hence, KCL is satisfied. The discrepancy is due to some resistance in the wires and resistor tolerance.

$$I_{R2} =$$

SAMPLE

The measure within 5% to wires and resistor tolerances.

C. Bridge Circuit

- Using the principle of voltage division show that for the bridge circuit shown in Figure # 8, $R_x = \frac{R_2 R_3}{R_1}$, if the voltage between points **p** and **q** is zero. When points **p** and **q** are at the same potential, the voltage across the meter (either volt

We can see that the voltage across R3, and R2 and Rx) is the same. The voltage between p and q is zero. Applying the voltage

SAMPLE

$$v_0 = \left(\frac{1}{1 + \frac{R_1}{R_2}} \right)$$

when $v_s = 0$, the
and we have:

$$\frac{R_1}{R_3} = \frac{R_2}{R_x}$$

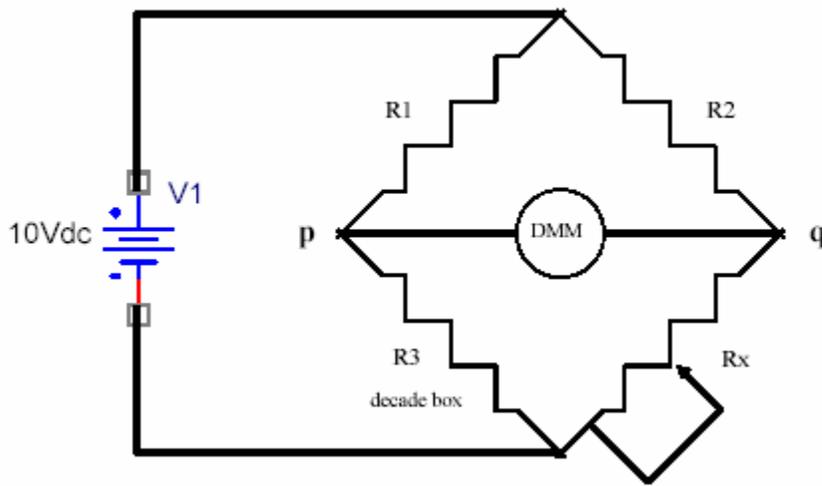


Figure #8. Bridge Circuit

2. Construct the bridge circuit with a decade box for R3 and a potentiometer for Rx and the pot shaft.
3. Turn the power on.
4. Monitor the voltage across the decade box resistor as you vary the potentiometer resistance. Based on the formula given in step 1, find Rx.



We adjust the value of the decade box to 4,601 Ω instead of 3,000 Ω . Applying the formula, we have:

$$R_x = \frac{R_2 R_3}{R_1} = \frac{4.7 \text{ k}\Omega * 4.6 \text{ k}\Omega}{2.2 \text{ k}\Omega} = 9.82 \text{ k}\Omega.$$

- Carefully remove the pot from the circuit without changing its shaft position. Now measure the resistance R_x using the ohmmeter and compare with the value obtained from the potentiometer. Note any discrepancies. A number of unknown resistors are included in the kit. Measure the resistance of them.

The measured resistance of the potentiometer is R_x . This represents the potentiometer's resistance at the potentiometer's fragility. The potentiometer is, in my opinion, most likely a sensitive potentiometer. A mistake in our



SAMPLE

Conclusion

In this lab experiment we verified KVL and KCL. We also tried to verify KVL and KCL.

In Part A we built a voltage divider. At the same time, we confirmed KVL and KCL. We built a fixed voltage divider and confirmed that it agreed with the theoretical values.

In Part B, using a current source, we verified KCL and the current divider rule.

In Part C we built a bridge circuit. We built a balanced bridge.



SAMPLE

Reference




Hu, Dr. Sung C, and Klingenberg, Larry "ENGR 206 Electric Circuits and Instrumentation: Laboratory Manual" April 2002

Attachments: Lab Notes

Tuesd.
2/19

Eng 206.

- * Intro to PSpice
- * Lab #3

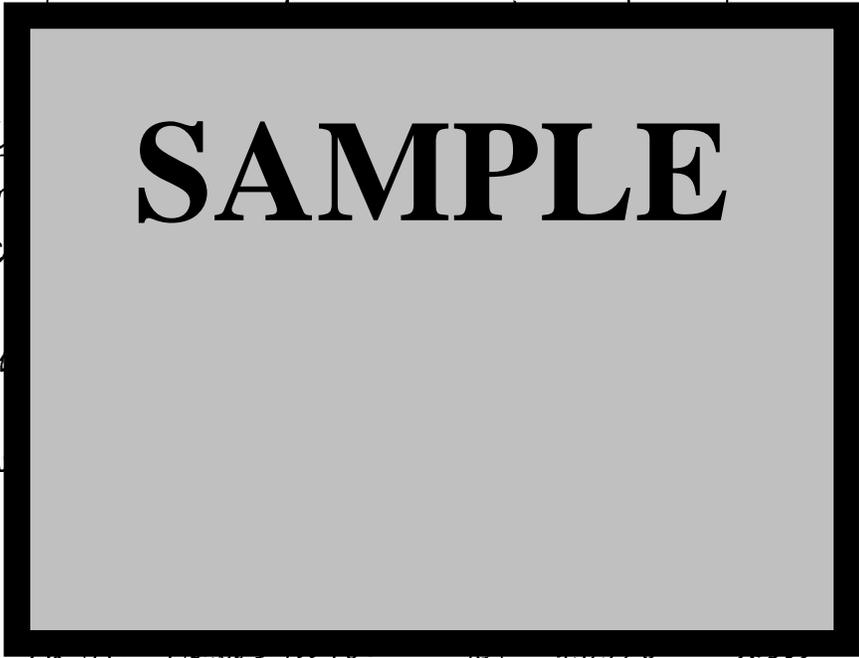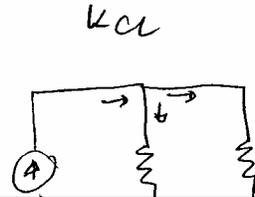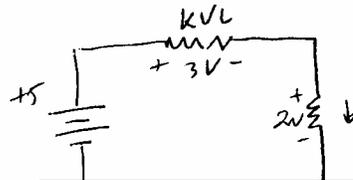

Lab 1

A. Vo

ac

ac

ker

⑤

R_2

R_1

$$V_0 = \frac{10V}{11.00} = 0.90909V$$

⊗

$R_2 = 10k\Omega$

$R_1 = 1k\Omega$

$$V_0^{R_2} = 9.90909V$$

$$V_0^{R_1} = 0.909091V \text{ across } R_1$$

$R_1 = 99.455mV = -99.457mV$

$R_2 = 9.9064V = -9.9025V$

$$V_0^{R_1} = 0.09901$$

D. Current Division

Adjusted to 50.139 μ A DC

④



SAMPLE

⑤ $I_{R2} =$

⑥ Leave $R_1 = 10$
Adjust to 50
 ~~$I_{R2} = 26.16$~~

$I_{R2} = 6.88$

$I_{R1} = 47.1$


C. Bridge circuit

Box at 4601 Ω not 3k Ω

$$R_x = \frac{R_2 R_3}{R_1} = 9.827 \text{ k}\Omega$$

Measured $R_x = 7.1058 \text{ k}\Omega$

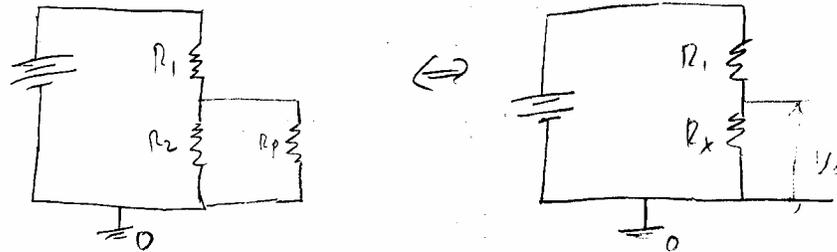ⓧ Potentiometer $10\text{ k}\Omega$
 $V_{\text{max}} = 10$
 $V_{\text{min}} = 0$
 Ⓞ $V_0 = 5$
 $V_0' = 6$
 $V_0' =$
 10V



$$R_x = \frac{10}{3} \text{ k}\Omega$$

$$V_0' = 10V \cdot \frac{R_x}{R_1 + R_x} = \frac{10 \cdot \frac{10}{3}}{3.3 + 5} = 4.0616$$

measured $V_0 = 3.9590$